

Фазоры комплексных напряжений ветвей приемника

$$U_{12} = \dot{U}_1 = -0.57 - j1.06 \quad 4 \angle -2.68^\circ \rightarrow 1.425$$

$$U_{23} = \dot{U}_{X12} = j1.885 \quad (-0.62 - j1.06) = 2.126$$

$$U_{34} = \dot{U}_{X23} = j0.67226 \quad (-0.62 - j1.06) = 1.96 \angle 45.92^\circ$$

$$U_{45} = \dot{U}_2 = 0.57 - j0.29 \quad 16 \angle 10.23^\circ \rightarrow 4.71$$

$$U_{56} = \dot{U}_{L1} = 0.4558 \quad (0.57 - j0.29) = 10.18 \angle 23.17^\circ$$

$$U_{67} = \dot{U}_{L2} = 0.90946 \quad (0.57 - j0.29) = 26.79 \angle 60.92^\circ$$

$$U_7 = \dot{U}_{R3} = 1.34 - j0.77 \quad 17 \angle 22.72^\circ \rightarrow 3.06$$

$$U_8 = \dot{U}_{X13} = 2.1991 \quad (1.34 - j0.77) = 16.89 \angle 29.46^\circ$$

$$U_{20} = \dot{U}_{L3} = j0 \quad (-1.34 - j0.77) = -0 + j0$$