

Фиксируем комплексные напряжения ветвей приемника

$$\begin{aligned}
 U_{12} &= I_1 R_1 = 0.13 - j0.365 \quad 6 \quad 0.78 - j2.188 \\
 U_{23} &= -jX_{L1} I_1 = j0.377 \quad (0.13 - j0.365) \quad 1.374 + j0.49 \\
 U_{34} &= -jX_{C1} I_1 = -j6.366 \quad (0.13 - j0.365) \quad -2.321 - j0.83 \\
 U_{45} &= I_2 R_2 = 0.87 - j2.08 \quad 25 = 2.173 - j5.195 \\
 U_{56} &= -jX_{L2} I_2 = j0 \quad (0.87 - j2.08) = 0 + j0 \\
 U_{67} &= -jX_{C2} I_2 = -j10.61 \quad (0.87 - j2.08) = -2.205 - j9.22 \\
 U_{78} &= I_3 R_3 = -0.74 - j1.57 \quad 32 \quad -2.365 - j5.017 \\
 U_{89} &= -jX_{L3} I_3 = -j78.54 \quad (-0.74 - j1.57) = 12.315 - j58.04 \\
 U_{97} &= -jX_{C3} I_3 = -j63.662 \quad (-0.74 - j1.57) = -99.82 + j47.05
 \end{aligned}$$