

Фазоры комплексных напряжений ветвей приемника

$$U_{12} = I_1 R_1 = 0.13 - j3.65 \quad 6 = 0.78 - j21.88$$

$$U_{23} = jX_{L1} I_1 = j3.77 (0.13 - j3.65) = 13.74 + j0.49$$

$$U_{34} = -jX_{C1} I_1 = -j6.366 (0.13 - j3.65) = -23.21 - j0.83$$

$$U_{45} = I_2 R_2 = 0.87 - j2.08 \quad 25 = 21.73 - j51.95$$

$$U_{56} = jX_{L2} I_2 = j0 (0.87 - j2.08) = 0 + j0$$

$$U_{67} = -jX_{C2} I_2 = -j10.61 (0.87 - j2.08) = -22.05 - j9.22$$

$$U_{48} = I_3 R_3 = -0.74 - j1.57 \quad 32 = -23.65 - j50.17$$

$$U_{19} = jX_{L3} I_3 = j78.54 (-0.74 - j1.57) = 123.15 - j58.04$$

$$U_{97} = -jX_{C3} I_3 = -j63.662 (-0.74 - j1.57) = -99.82 + j47.05$$