

выполним эквивалентное преобразование схемы и определим комплексные параметры цепи

$$\omega = 2\pi f = 2\pi \cdot 50 = 314\,1593 \text{ rad/s}$$

$$E_1 = \frac{E_{m1}}{\sqrt{2}} e^{j\varphi_1} = 17\,678 e^{j25^\circ} \text{ V}$$

$$J_2 = \frac{J_{m2}}{\sqrt{2}} e^{j\varphi_2} = 10\,607 e^{j15^\circ} \text{ A}$$

$$E_2 = \frac{J_2}{G_{m2}} = \frac{10\,225 + j2\,735}{0.1} = 102\,45 + j27\,45 \text{ V}, R_{m2} = \frac{1}{G_{m2}} = \frac{1}{0.1} = 10 \Omega$$

$$E_{eq} = E_1 - E_2 = 16\,02 + j7\,47 - (102\,45 + j27\,45) = -86\,43 - j19\,98 \text{ V}$$

$$Z_{c1,m} = (R_{m1} + R_{m2}) + jX_{Lm1} = (5 + 10) + j2 = 15 + j2 \Omega = 15.13 e^{j7.59 \text{ deg}}$$

Рассчитаем эквивалентные сопротивления ветвей приемника

$$X_{L1} = \omega L_1 = 314\,1593 \cdot 0.006 = 1\,885 \Omega, X_{C1} = \frac{1}{\omega C_1} = \frac{1}{314\,1593 \cdot 0.0000037} = 67\,726 \Omega$$

$$X_{L2} = \omega L_2 = 314\,1593 \cdot 0.11 = 34\,558 \Omega, X_{C2} = \frac{1}{\omega C_2} = \frac{1}{314\,1593 \cdot 0.0000035} = 90\,946 \Omega$$

$$X_{L3} = \omega L_3 = 314\,1593 \cdot 0.07 = 21\,991 \Omega, X_{C3} = \frac{1}{\omega C_3} = \frac{1}{314\,1593 \cdot 0.000001} = 0 \Omega$$

$$Z_1 = R_1 + jX_{L1} - jX_{C1} = 4 + j1\,885 - j67\,726 = 4 - j65\,84$$

$$Z_2 = R_2 + jX_{L2} - jX_{C2} = 16 + j34\,558 - j90\,946 = 16 - j56\,39$$

$$Z_3 = R_3 + jX_{L3} - jX_{C3} = 17 + j21\,991 - j0 = 17 + j21\,99$$

Находим эквивалентное сопротивление нагрузки и полное сопротивление цепи

$$Z_{23} = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(16 - j56\,39)(17 + j21\,99)}{33 - j344} = 31.15 + j14.08$$

$$Z_{c1,load} = Z_1 + Z_{23} = 4 - j65.84 + (31.15 + j14.08) = 35.15 - j51.76$$

$$Z_m = Z_{c1,m} + Z_{c1,load} = 15 + j2 + (35.15 - j51.76) = 50.15 - j49.76$$

Определим значения токов

$$I_1 = \frac{E_{c1}}{Z_m} = \frac{-86.43 - j19.98}{50.15 - j49.76} = -0.67 - j1.06 \text{ A}$$

$$I_2 = I_1 \frac{Z_3}{Z_2 + Z_3} = -0.67 - j1.06 \cdot \frac{17 + j21.99}{33 - j344} = 0.67 - j0.29 \text{ A}$$

$$I_3 = I_1 - I_2 = -0.67 - j1.06 - (0.67 - j0.29) = -1.34 - j0.77 \text{ A}$$

Выполняем проверку расчетов по закону Кирхгофа

$$\Delta I = 0 + j0, \Delta U_1 = 0 + j0, \Delta U_2 = -0 + j0$$

$$\varepsilon_{KCL} = 0\%, \varepsilon_{KVL} = 0\%$$