

Фазоры и комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = -0.67 - j1.064 = -2.68 - j4.25$$

$$U_{23} = jX_{L1} I_1 = j1.885 (-0.67 - j1.06) = 2 - j1.26$$

$$U_{34} = -jX_{C1} I_1 = -j67.726 (-0.67 - j1.06) = -71.96 + j45.32$$

$$U_{45} = I_2 R_2 = 0.67 - j0.2916 = 10.73 - j4.71$$

$$U_{56} = jX_{L2} I_2 = j34.558 (0.67 - j0.29) = 10.18 + j23.17$$

$$U_{67} = -jX_{C2} I_2 = -j90.946 (0.67 - j0.29) = -26.79 - j60.97$$

$$U_{78} = I_3 R_3 = -1.34 - j0.7717 = -22.77 - j13.06$$

$$U_{89} = jX_{L3} I_3 = j21.991 (-1.34 - j0.77) = 16.89 - j29.46$$

$$U_{97} = -jX_{C3} I_3 = -j0 (-1.34 - j0.77) = -0 + j0$$