

Фиксируем комплексные напряжения ветвей приемника

$$\bar{U}_{12} = I_1 R_1 = (0.67 - j1.06) \cdot 4 = 2.68 - j4.25$$

$$\bar{U}_{23} = I_2 X_{L1} I_1 = 1.1885 \cdot (-0.67 - j1.06) = -0.79 - j1.26$$

$$\bar{U}'_{34} = -jX_{L1} I_1 = -j67.726 \cdot (-0.67 - j1.06) = 71.96 + j45.32$$

$$\bar{U}_{45} = I_2 R_2 = (0.67 - j0.29) \cdot 16 = 10.73 - j4.71$$

$$\bar{U}_{56} = I_2 X_{L2} I_2 = 1.34558 \cdot (0.67 - j0.29) = 0.90 + j0.23$$

$$\bar{U}'_6 = -jX_{L2} I_2 = -j90.946 \cdot (0.67 - j0.29) = -26.79 - j60.97$$

$$\bar{U}_{48} = I_3 R_3 = (-1.34 - j0.77) \cdot 17 = -22.77 - j13.06$$

$$\bar{U}'_{89} = -jX_{L3} I_3 = -j21.991 \cdot (-1.34 - j0.77) = 16.89 - j29.46$$

$$\bar{U}'_9 = -jX_{L3} I_3 = -j0 \cdot (-1.34 - j0.77) = 0 + j0$$