

Выполним эквивалентное преобразование схемы и определим комплексные параметры цепи

$$\omega = 2\pi f = 2\pi \cdot 50 = 314 \, 1593 \, \text{rad/s}$$

$$E_1 = \frac{E_{m1}}{\sqrt{2}} e^{j\varphi_1} = 17 \, 678 e^{j25^\circ} \, \text{V}$$

$$J_2 = \frac{J_{m2}}{\sqrt{2}} e^{j\varphi_2} = 10 \, 607 e^{j15^\circ} \, \text{A}$$

$$E_2 = \frac{J_2}{G_{m2}} = \frac{10 \, 28 + j2 \, 75}{0.1} = 102 \, 45 + j27 \, 45 \, \text{V}, R_{m2} = \frac{1}{G_{m2}} = \frac{1}{0.1} = 10 \, \Omega$$

$$E_{eq} = E_1 - E_2 = 16 \, 02 + j7 \, 47 - (102 \, 45 + j27 \, 45) = -86 \, 43 - j19 \, 98 \, \text{V}$$

$$Z_{cг, m} = (R_{m1} + R_{m2}) + jX_{Lm1} = (5 + 10) + j2 = 15 + j2 \, \Omega = 15 \, 13 e^{j7 \, 59 \, \text{deg}}$$

Рассчитаем эквивалентные сопротивления ветвей цепи

$$X_{L1} = \omega L_1 = 314 \, 1593 \cdot 0 \, 006 = 1 \, 885 \, \Omega, X_{C1} = \frac{1}{\omega C_1} = \frac{1}{314 \, 1593 \cdot 0 \, 000047} = 67 \, 726 \, \Omega$$

$$X_{L2} = \omega L_2 = 314 \, 1593 \cdot 0 \, 11 = 34 \, 558 \, \Omega, X_{C2} = \frac{1}{\omega C_2} = \frac{1}{314 \, 1593 \cdot 0 \, 000035} = 90 \, 946 \, \Omega$$

$$X_{L3} = \omega L_3 = 314 \, 1593 \cdot 0 \, 07 = 21 \, 991 \, \Omega, X_{C3} = \frac{1}{\omega C_3} = \frac{1}{314 \, 1593 \cdot 0} = 0 \, \Omega$$

$$Z_1 = R_1 + jX_{L1} - jX_{C1} = 4 + j1 \, 885 - j67 \, 726 = 4 - j65 \, 84$$

$$Z_2 = R_2 + jX_{L2} - jX_{C2} = 16 + j34 \, 558 - j90 \, 946 = 16 - j56 \, 39$$

$$Z_3 = R_3 + jX_{L3} - jX_{C3} = 17 + j21 \, 991 - j0 = 17 + j21 \, 99$$

Находим эквивалентное сопротивление нагрузки и полное сопротивление цепи

$$Z_{23} = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(16 - j56 \, 39)(17 + j21 \, 99)}{33 - j344} = 31 \, 15 + j14 \, 08$$

$$Z_{cг, load} = Z_1 + Z_{23} = 4 - j65 \, 84 + (31 \, 15 + j14 \, 08) = 35 \, 15 - j51 \, 76$$

$$Z_m = Z_{cг, m} + Z_{cг, load} = 15 + j2 + (35 \, 15 - j51 \, 76) = 50 \, 15 - j49 \, 76$$

Определим значения токов

$$I_1 = \frac{E_1}{Z_m} = \frac{-86 \, 43 - j19 \, 98}{50 \, 15 - j49 \, 76} = -0 \, 67 - j1 \, 06 \, \text{A}$$

$$I_2 = I_1 \frac{Z_3}{Z_2 + Z_3} = -0 \, 67 - j1 \, 06 \cdot \frac{17 + j21 \, 99}{33 - j344} = 0 \, 67 - j0 \, 29 \, \text{A}$$

$$I_3 = I_1 - I_2 = -0 \, 67 - j1 \, 06 - (0 \, 67 - j0 \, 29) = -1 \, 34 - j0 \, 77 \, \text{A}$$

Выполняем проверку расчетов по закону Кирхгофа

$$\Delta I = 0 + j0, \Delta U_1 = 0 + j0, \Delta U_2 = -0 + j0$$

$$\varepsilon_{KCL} = 0\%, \varepsilon_{KVL} = 0\%$$