

Фиксируем комплексные напряжения ветвей приемника

$$\begin{aligned} U_{12} &= I_1 R_1 = -2.17 - j1.37 \text{ В} = -8.66 - j5.47 \text{ В} \\ U_{23} &= -jX_{l1} I_1 = j4.084 (-2.17 - j1.37) = 5.59 - j8.84 \text{ В} \end{aligned}$$

$$\begin{aligned} U_{34} &= -jX_{l1} I_1 = -j0. (-2.17 - j1.37) = 0 + j0 \text{ В} \\ U_{45} &= I_2 R_2 = -2.12 + j0.05 \text{ В} = -31.8 - j0.77 \text{ В} \end{aligned}$$

$$\begin{aligned} U_{56} &= jX_{l2} I_2 = j21.991 (-2.12 + j0.05) = -11.3 - j46.62 \text{ В} \\ U_{67} &= -jX_{l2} I_2 = -j12.732 (-2.12 + j0.05) = 0.65 + j26.99 \text{ В} \end{aligned}$$

$$\begin{aligned} U_{48} &= I_3 R_3 = -0.05 - j1.42 \text{ В} = -0.64 - j19.87 \text{ В} \\ U_{89} &= -jX_{l3} I_3 = -j34.558 (-0.05 - j1.42) = 49.06 - j1.58 \text{ В} \\ U_{97} &= -jX_{l3} I_3 = -j56.841 (-0.05 - j1.42) = -80.69 - j2.6 \text{ В} \end{aligned}$$