

Всполним эквивалентное преобразование схемы и определим комплексные параметры цепи

$$\omega = 2\pi f = 2\pi \cdot 500 = 3141,5927 \text{ rad/s}$$

$$E_1 = \frac{E_{m1}}{\sqrt{2}} e^{j\varphi_1} = 29,698 e^{-j40^\circ} \text{ V}$$

$$J_1 = \frac{J_{m1}}{\sqrt{2}} e^{j\varphi_1} = 14,142 e^{j30^\circ} \text{ A}$$

$$E_2 = \frac{J_1}{G_{m2}} = \frac{12,5 + j7,07}{0,15} = 81,65 + j47,14 \text{ V}, R_{m2} = \frac{1}{G_{m2}} = \frac{1}{0,15} = 6,667 \Omega$$

$$E_{eq} = E_1 - E_2 = 29,698 - j19,09 - (81,65 + j47,14) = -58,95 - j66,23 \text{ V}$$

$$Z_{eq, n} = (R_{m1} + R_{m2}) + jX_{Lm1} = (8 + 6,667) + j6 = 14,67 + j6 \Omega = 15,85 e^{j22,25^\circ} \text{ deg}$$

Рассчитаем эквивалентные сопротивления ветвей приемника

$$X_{L1} = \omega L_1 = 3141,5927 \cdot 0,0013 = 4,084 \Omega, X_{C1} = \frac{1}{\omega C_1} = \frac{1}{3141,5927 \cdot 10^{-6}} = 0 \Omega$$

$$X_{L2} = \omega L_2 = 3141,5927 \cdot 0,007 = 21,991 \Omega, X_{C2} = \frac{1}{\omega C_2} = \frac{1}{3141,5927 \cdot 0,0000075} = 12,732 \Omega$$

$$X_{L3} = \omega L_3 = 3141,5927 \cdot 0,011 = 34,558 \Omega, X_{C3} = \frac{1}{\omega C_3} = \frac{1}{3141,5927 \cdot 0,0000056} = 56,841 \Omega$$

$$Z_1 = R_1 + jX_{L1} - jX_{C1} = 4 + j4,084 - j0 = 4 + j4,08$$