

Фазоры и комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = 6 \angle 0^\circ \cdot 2 \angle 0^\circ = 12 \angle 0^\circ$$

$$U_{23} = I_2 R_2 = 1 \angle 27^\circ \cdot 2 \angle 0^\circ = 2 \angle 27^\circ$$

$$U_{04} = I_4 R_4 = 1 \angle 83.1^\circ \cdot 2 \angle 0^\circ = 2 \angle 83.1^\circ$$

$$U_{45} = I_5 R_5 = 0.7 \angle 21.1^\circ \cdot 14 \angle 0^\circ = 9.8 \angle 21.1^\circ$$

$$U_{56} = I_6 R_6 = 1.4 \angle 0^\circ \cdot 7 \angle 0^\circ = 9.8 \angle 0^\circ$$

$$U_{67} = I_7 R_7 = 1.9 \angle 89^\circ \cdot 10 \angle 0^\circ = 19 \angle 89^\circ$$

$$U_{48} = I_8 R_8 = 5.45 \angle 29.9^\circ \cdot 16 \angle 0^\circ = 87.2 \angle 29.9^\circ$$

$$U_{89} = I_9 R_9 = 1.885 \angle 45^\circ \cdot 54 \angle 0^\circ = 102.09 \angle 45^\circ$$

$$U_{90} = I_{10} R_{10} = 0 \angle 0^\circ \cdot 0 \angle 0^\circ = 0 \angle 0^\circ$$