

Фазоры и комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = 6 \angle 0^\circ \cdot 22 \angle 8^\circ = 49.25 \angle 17.2^\circ$$

$$U_{23} = I_2 X_L = 1.257 \angle -6.6^\circ \cdot 22 \angle 2^\circ = 27.9 \angle -7.4^\circ$$

$$U_{04} = I_4 X_C = 1.831 \angle -6.6^\circ \cdot 22 \angle 2^\circ = 20.56 \angle -9.5^\circ$$

$$U_{45} = I_2 R_2 = 0.71 \angle 14^\circ \cdot 21 \angle -9^\circ = 14.9 \angle 5^\circ$$

$$U_{56} = I_2 X_L = 1.4 \angle 17^\circ \cdot 21 \angle -5^\circ = 29.4 \angle 12^\circ$$

$$U_{67} = I_2 X_C = 1.9789 \angle -0.71 \angle 21^\circ = 20.735 \angle -28.2^\circ$$

$$U_{48} = I_3 R_3 = 5.45 \angle 29^\circ \cdot 16 \angle -87^\circ = 87.16 \angle -58^\circ$$

$$U_{89} = I_3 X_C = 1.885 \angle -5.45 \angle 29^\circ = 56.45 \angle -102.68^\circ$$

$$U_{90} = I_3 R_3 = 1 \angle -5.45 \angle 29^\circ = 0 \angle 0^\circ$$