

Фазоры комплексные напряжения ветвей приемника

$$U_{12} = I_2 R_1 = -0.91 + j1.59 \quad 18^\circ = -16.32 + j28.7$$

$$U_{22} = jX_{L2} I_2 = j7.54 (-0.91 + j1.59) = -2.02 - j6.84$$

$$U_{14} = jX_{M2} I_2 = j9.095 (-0.91 + j1.59) = -4.5 + j8.25$$

$$U_{45} = I_2 R_2 = -0.43 + j0.94 \quad 22^\circ = -9.52 + j20.65$$

$$U_{56} = jX_{L2} I_2 = j4.712 (-0.43 + j0.94) = -4.42 - j2.04$$

$$U_{67} = jX_{M2} I_2 = j7.074 (-0.43 + j0.94) = 6.64 + j3.06$$

$$U_{48} = I_2 R_3 = -0.47 + j0.66 \quad 27^\circ = -12.8 + j17.2 \quad U_{89} = jX_{L3} I_2 = j0 (-0.47 + j0.66) = 0 + j0$$

$$U_{97} = jX_{M3} I_2 = j8.377 (-0.47 + j0.66) = 5.49 + j3.92$$