

Фиксируем комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = -0.91 + j1.59 \quad 18 = -16.32 + j28.7$$

$$U_{20} = jX_{L1} I_1 = j7.54 (-0.91 + j1.59) = -12.02 - j6.84$$

$$U_{34} = -jX_{C1} I_1 = -j9.095 (-0.91 + j1.59) = 14.5 + j8.25$$

$$U_{45} = I_2 R_2 = -0.43 + j0.94 \quad 22 = -9.52 + j20.65$$

$$U_{56} = jX_{L2} I_2 = j4.712 (-0.43 + j0.94) = -4.42 - j2.04$$

$$U_{67} = -jX_{C2} I_2 = -j7.074 (-0.43 + j0.94) = 6.64 + j3.06$$

$$U_{48} = I_3 R_3 = -0.47 + j0.66 \quad 27 = -12.8 + j17.7, \quad U_{89} = jX_{L3} I_3 = j0 (-0.47 + j0.66) = 0 + j0$$

$$U_{97} = -jX_{C3} I_3 = -j8.377 (-0.47 + j0.66) = 5.49 + j3.97$$