

Выполним эквивалентное преобразование схемы и определим комплексные параметры цепи

$$\omega = 2\pi f = 2\pi \cdot 500 = 3141.5927 \text{ рад/с}$$

$$E_N = \frac{E_{m1}}{\sqrt{2}} e^{j\varphi_1} = 29.698 e^{-j40^\circ} \text{ В}$$

$$J_2 = \frac{J_{m2}}{\sqrt{2}} e^{j\varphi_2} = 14.142 e^{j30^\circ} \text{ А}$$

$$E_2 = \frac{J_2}{G_{m2}} = \frac{14.142 e^{j30^\circ}}{0.15} = 81.65 + j47.14 \text{ В}, R_{m2} = \frac{1}{G_{m2}} = \frac{1}{0.15} = 6.667 \Omega$$

$$E_{eq} = E_1 - E_2 = 22.25 - j19.09 - (81.65 + j47.14) = -58.9 - j66.23 \text{ В}$$

$$Z_{eq, n} = (R_{m1} + R_{m2}) + jX_{Lm1} = (8 + 6.667) + j6 = 14.67 + j6 \Omega = 15.85 e^{j22.25^\circ} \text{ deg}$$

Рассчитаем эквивалентные сопротивления ветвей приемника

$$X_{L1} = \omega L_1 = 3141.5927 \cdot 0.0013 = 4.084 \Omega, X_{C1} = \frac{1}{\omega C_1} = \frac{1}{3141.5927 \cdot 0.00005} = 0 \Omega$$

$$X_{L2} = \omega L_2 = 3141.5927 \cdot 0.007 = 21.991 \Omega, X_{C2} = \frac{1}{\omega C_2} = \frac{1}{3141.5927 \cdot 0.000025} = 12.732 \Omega$$

$$X_{L3} = \omega L_3 = 3141.5927 \cdot 0.011 = 34.558 \Omega, X_{C3} = \frac{1}{\omega C_3} = \frac{1}{3141.5927 \cdot 0.000056} = 56.841 \Omega$$

$$Z \quad R \quad \vee \quad \chi \quad < \quad < 0.8 \quad 0 \quad < \quad < 0.8$$