

Фиксируем комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = -2.17 - j1.37 \text{ A} = -8.66 - j5.47 \text{ V}$$

$$U_{20} = jX_{L1} I_1 = j4.084 (-2.17 - j1.37) = 5.59 - j8.84 \text{ V}$$

$$U_{34} = -jX_{C1} I_1 = -j0 (-2.17 - j1.37) = -0 + j0 \text{ V}$$

$$U_{45} = I_2 R_2 = -2.12 + j0.05 \text{ A} = -31.8 + j0.77 \text{ V}$$

$$U_{56} = jX_{L2} I_2 = j21.991 (-2.12 + j0.05) = -1.13 - j46.62 \text{ V}$$

$$U_{67} = -jX_{C2} I_2 = -j12.732 (-2.12 + j0.05) = 0.65 + j26.99 \text{ V}$$

$$U_{48} = I_3 R_3 = -0.05 - j1.42 \text{ A} = -0.64 - j19.87 \text{ V}$$

$$U_{89} = jX_{L3} I_3 = j34.558 (-0.05 - j1.42) = 49.06 - j1.58 \text{ V}$$

$$U_{97} = -jX_{C3} I_3 = -j56.841 (-0.05 - j1.42) = -80.69 + j2.6 \text{ V}$$