

Фиксируем комплексные напряжения ветвей приемника

$$\mathcal{U}_{12} = I_1 R_1 = -0.91 + j1.59 \quad 18^\circ \quad -16.32 + j28.7$$

$$\mathcal{U}_{23} = jX_{l1} I_1 = j7.54 (-0.91 + j1.59) = -12.02 - j6.84$$

$$\mathcal{U}_{34} = -jX_{l1} I_1 = -j9.095 (-0.91 + j1.59) = 14.5 + j8.25$$

$$\mathcal{U}_{45} = I_2 R_2 = -0.43 + j0.94 \quad 22^\circ = -9.52 + j20.65$$

$$\mathcal{U}_{56} = jX_{l2} I_2 = j4.712 (-0.43 + j0.94) = -4.42 - j2.04$$

$$\mathcal{U}_{67} = -jX_{l2} I_2 = -j7.074 (-0.43 + j0.94) = 6.64 + j3.06$$

$$\mathcal{U}_{48} = I_3 R_3 = -0.47 + j0.66 \quad 27^\circ = -12.8 + j17.7 \quad \mathcal{U}_{89} = jX_{l3} I_3 = j0 \quad (-0.47 + j0.66) = 0 + j0$$

$$\mathcal{U}_{97} = -jX_{l3} I_3 = -j8.377 (-0.47 + j0.66) = 5.49 + j3.97$$