

Фиксируем комплексные напряжения ветвей приемника

$$\bar{U}_{12} = I_1 R_1 = -0.67 - j1.06 \quad 4 \quad -2.68 - j4.25$$

$$\bar{U}_{23} = jX_{L1} I_1 = j1.885 \quad (-0.67 - j1.06) \quad 2 - j1.26$$

$$\bar{U}'_{34} = -jX_{L1} I_1 = -j67.726 \quad (-0.67 - j1.06) \quad -71.96 + j45.32$$

$$\bar{U}_{45} = I_2 R_2 = 0.67 - j0.29 \quad 16 = 10.73 - j4.71$$

$$\bar{U}_{56} = jX_{L2} I_2 = j34.558 \quad (0.67 - j0.29) = 10.18 + j23.17$$

$$\bar{U}'_6 = -jX_{L2} I_2 = -j90.946 \quad (0.67 - j0.29) = -26.79 - j60.97$$

$$\bar{U}_{48} = I_3 R_3 = -1.34 - j0.77 \quad 17 \quad -22.77 - j13.06$$

$$\bar{U}'_{89} = jX_{L3} I_3 = j21.991 \quad (-1.34 - j0.77) = 16.89 - j29.46$$

$$\bar{U}'_9 = -jX_{L3} I_3 = -j0 \quad (-1.34 - j0.77) = -0 + j0$$