

Фиксируем комплексные напряжения ветвей приемника

$$\begin{aligned}
 \dot{U}_{12} &= I_1 R_1 = -2.17 - j1.37 \quad 4 \quad -8.66 - j5.47 \\
 \dot{U}_{23} &= jX_{l1} I_1 = j4.084 \quad (-2.17 - j1.37) = 5.59 - j8.84 \\
 \dot{U}_{34} &= -jX_{l1} I_1 = -j0 \quad (-2.17 - j1.37) = -0.170 \\
 \dot{U}_{45} &= I_2 R_2 = -2.12 + j0.05 \quad 15 = -31.8 \quad j0.77 \\
 \dot{U}_{56} &= jX_{l2} I_2 = j21.991 \quad (-2.12 + j0.05) = -1.13 - j46.62 \\
 \dot{U}_{67} &= -jX_{l2} I_2 = -j12.732 \quad (-2.12 + j0.05) = 0.65 + j26.99 \\
 \dot{U}_{48} &= I_3 R_3 = -0.05 - j1.42 \quad 14 \quad -0.64 - j19.87 \\
 \dot{U}_{89} &= jX_{l3} I_3 = j34.558 \quad (-0.05 - j1.42) = 49.06 - j1.58 \\
 \dot{U}_{97} &= -jX_{l3} I_3 = -j56.841 \quad (-0.05 - j1.42) = -80.69 \quad j2.6
 \end{aligned}$$