

Фиксируем комплексные напряжения ветвей приемника

$$\mathcal{U}_{12}' = I_1 R_1 = -6 \text{ } 16 - j2 \text{ } 22 \text{ } 8 = -49 \text{ } 25 - j17 \text{ } 73$$

$$\mathcal{U}_{23}' = jX_{l1} I_1 = j1 \text{ } 257 \text{ } (-6 \text{ } 16 - j2 \text{ } 22) = 2 \text{ } 79 - j7 \text{ } 74$$

$$\mathcal{U}_{34}' = -jX_{l1} I_1 = -j3 \text{ } 183 \text{ } 1 \text{ } (-6 \text{ } 16 - j2 \text{ } 22) = -70 \text{ } 56 \text{ } j195 \text{ } 97$$

$$\mathcal{U}_{45}' = I_2 R_2 = -0 \text{ } 71 - j5 \text{ } 21 \text{ } 14 = -9 \text{ } 93 - j72 \text{ } 96$$

$$\mathcal{U}_{56}' = jX_{l2} I_2 = j14 \text{ } 137 \text{ } (-0 \text{ } 71 - j5 \text{ } 21) = 73 \text{ } 67 - j10 \text{ } 03$$

$$\mathcal{U}_{67}' = -jX_{l2} I_2 = -j39 \text{ } 789 \text{ } (-0 \text{ } 71 - j5 \text{ } 21) = -207 \text{ } 35 + j28 \text{ } 22$$

$$\mathcal{U}_{48}' = I_3 R_3 = -5 \text{ } 45 + j2 \text{ } 99 \text{ } 16 = -87 \text{ } 16 + j47 \text{ } 91$$

$$\mathcal{U}_{89}' = jX_{l3} I_3 = j18 \text{ } 85 \text{ } (-5 \text{ } 45 - j2 \text{ } 99) = -56 \text{ } 45 - j102 \text{ } 68$$

$$\mathcal{U}_{97}' = -jX_{l3} I_3 = -j0 \text{ } (-5 \text{ } 45 + j2 \text{ } 99) = 0 \text{ } j0$$