

Фиксируем комплексные напряжения ветвей приемника

$$U_{12} = I_1 R_1 = -6.16 - j2.22 \cdot 8 = -49.25 - j17.73$$

$$U_{23} = jX_{L1} I_1 = j1.257 (-6.16 - j2.22) = 2.79 - j7.74$$

$$U_{34} = -jX_{C1} I_1 = -j31.831 (-6.16 - j2.22) = -70.56 + j195.97$$

$$U_{45} = I_2 R_2 = -0.71 - j5.21 \cdot 14 = -9.93 - j72.96$$

$$U_{56} = jX_{L2} I_2 = j14.137 (-0.71 - j5.21) = 73.67 - j10.03$$

$$U_{67} = -jX_{C2} I_2 = -j39.789 (-0.71 - j5.21) = -207.35 + j28.22$$

$$U_{48} = I_3 R_3 = -5.45 + j2.99 \cdot 16 = -87.16 + j47.91$$

$$U_{89} = jX_{L3} I_3 = j18.85 (-5.45 + j2.99) = -56.45 - j102.68$$

$$U_{97} = -jX_{C3} I_3 = -j0 (-5.45 + j2.99) = 0 + j0$$